



ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)

ORGANIZATION OF ISLAMIC COOPERATION (OIC)

DEPARTMENT OF ELECTRICAL AND ELECTRONIC
ENGINEERING

PROJECT REPORT

NAME

STUDENT ID

- | | |
|------------------------|-----------|
| 1. MD Wahiduzzaman | 200021228 |
| 2. Rahib Bin Hossain | 200021241 |
| 3. K. M. Sirazul Monir | 200021247 |
| 4. Feehad Kamal | 200021218 |
| 5. M.M.Sadman Shafi | 200021240 |

COURSE NO. : EEE 4504

DEPARTMENT : EEE

SECTION : B

Portable Power station

Introduction:

In a world that grapples with an ever-expanding energy demand, certain regions face unique challenges that demand innovative solutions. Bangladesh, a nation marked by its resilience and rapid development, frequently contends with power crises that impact both urban centers and rural communities. The need for reliable and accessible electricity in this context cannot be overstated.

Our project, the 'Portable Power Station,' takes cognizance of the pressing power issues that prevail in Bangladesh. With its ability to efficiently convert DC voltage to DC and AC voltage as well, our proposed solution emerges as a beacon of hope amidst these challenges. It is tailored to be not just a portable power source but a lifeline for those enduring power shortages.

The 'Portable Power Station' offers the promise of consistent and dependable electricity, whether it's for essential medical equipment in remote clinics, sustaining daily livelihoods in rural areas, or ensuring uninterrupted education in urban centers. By harnessing the power of efficient conversion, we aim to play a pivotal role in mitigating the power crisis that has plagued Bangladesh, ultimately contributing to the nation's development and the well-being of its people.

Feature:

The aim of our project was to provide power in rural areas where electricity was not readily available.


Our project provided electricity power in two forms which were mostly used:

1. 230V AC, and
2. 5V DC (USB,) from a single battery or solar panel (any 12V source).

The AC current could be used to power most medium to small devices such as small light bulbs, laptops, small fans, TVs, etc. On the other hand, 5V DC could be used to charge up mobiles or other devices that use USB. It featured a feedback system that maintained steady 5V DC at the output.

Technical details: This project has two parts. The first part is an inverter that generates 230V AC from 12V DC. The second part is a BUCK converter which generates steady 5V DC from 12V DC.

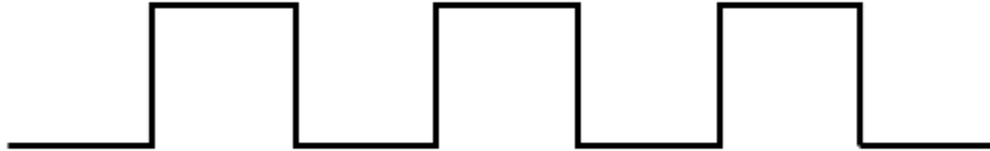Inverter: The AC current is alternating and always changing direction. So, by arranging two MOSFETs in such a way that one will turn on and supply current in one direction, and after a few moments it turns off and the other MOSFET turns on to supply DC current in the opposite direction - if we can do it 50 times a second, we get basically ac current. But it will be a square wave AC current.



Square Wave

In order to make it more usable, we can do the following ways:

- The first MOSFET turns on, second one turns off.
- Then two of them turn off.
- Then the second one turns on, first one turns off.
- Then two of them turn off.


The MOSFETs will be controlled by a Mosfet Driver which in this case we will be using BJT as Mosfet Driver. The on/off pulses will be provided by an Arduino.

If we implement this way, we get a modified square wave.




Modified Square wave

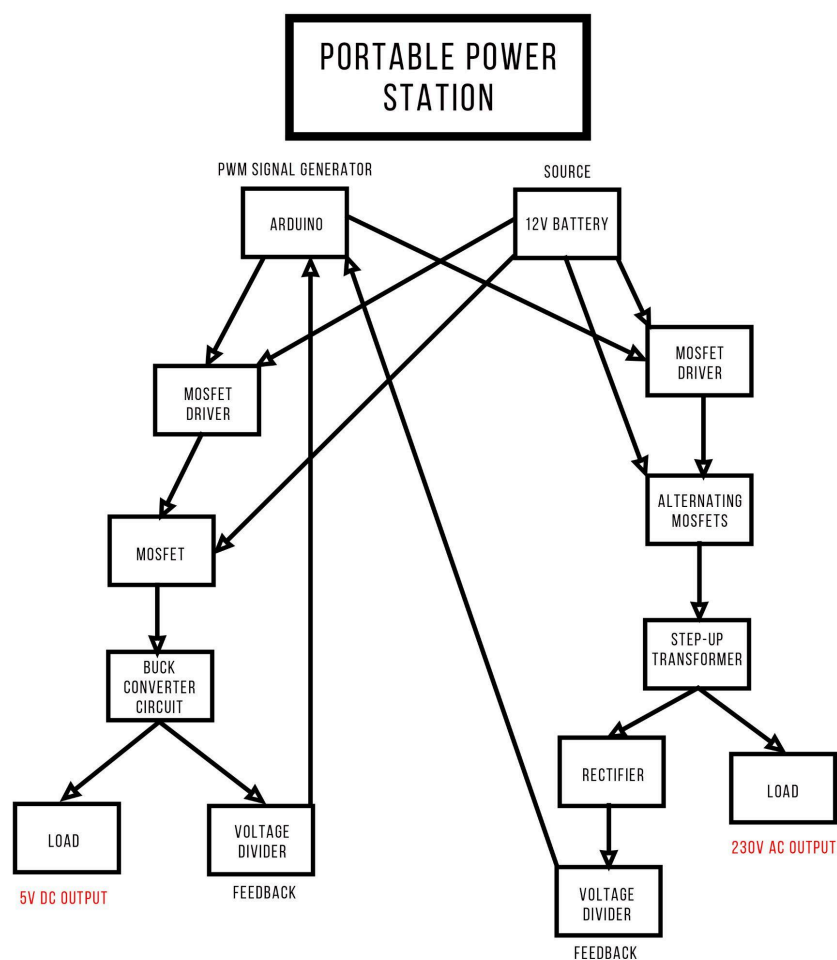After that, the current can be fed to a step-up transformer with appropriate coil ratio and power ratings to get 230V AC.



Circuit Diagram:

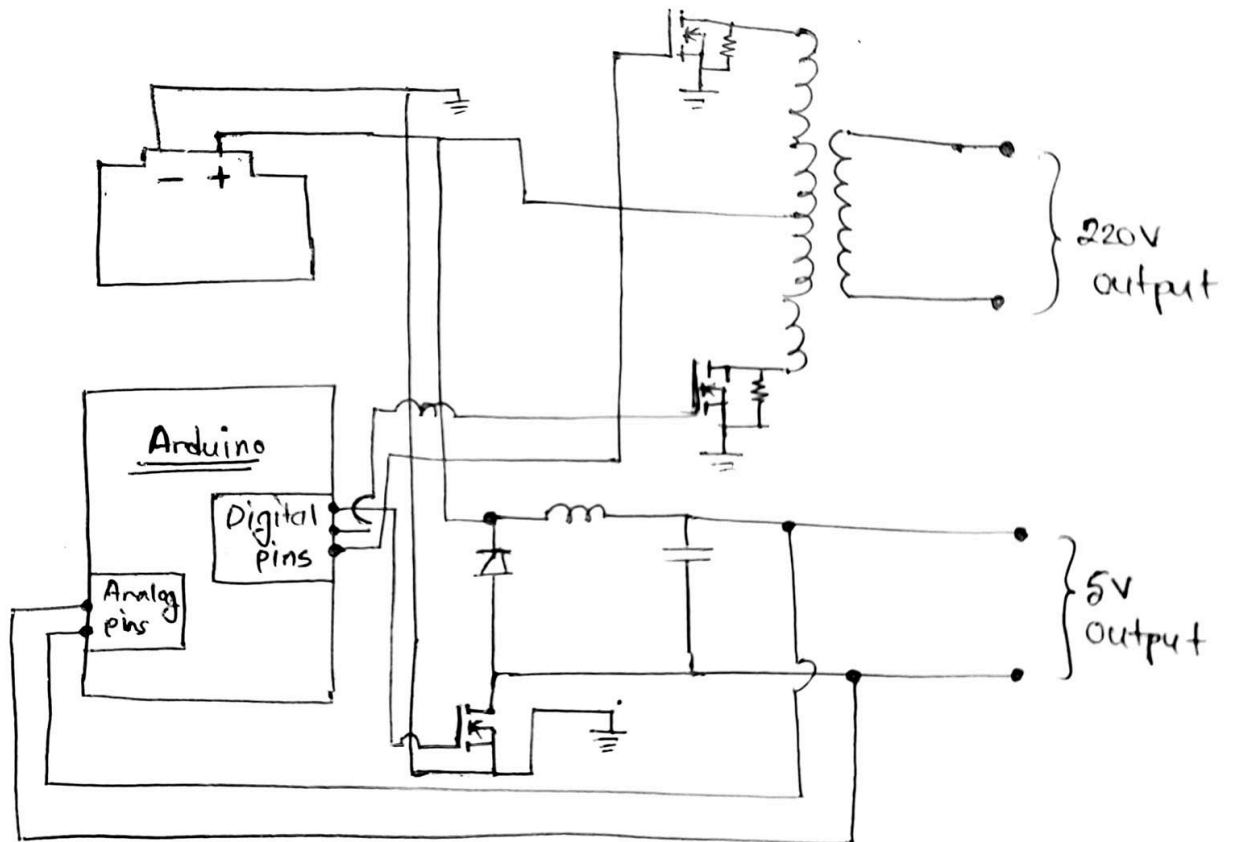

Implementation:

Arduino Code:

```
unsigned long previousMillis = 0;
const long interval = 10; // 20 ms for a 50 Hz PWM signal
int pwmState = 0; // 0 or 1 to alternate between pins 2 and 4
#define PWM_PIN 9
#define ANALOG_PIN_A0 A0
#define ANALOG_PIN_A1 A1

const int numReadings = 10;
int readingsA0[numReadings];
int readingsA1[numReadings];
int index = 0;
int totalA0 = 0;
int totalA1 = 0;
int a;
int x = 10;

void setup() {
  pinMode(2, OUTPUT);
  pinMode(4, OUTPUT);
  pinMode(PWM_PIN, OUTPUT);
  Serial.begin(9600);
  TCCR1B = TCCR1B & 0b11111000 | 0x01; // set timer 1 divisor to 1 for PWM
  frequency of 31372.55 Hz
}

void loop() {

  // Smooth out the reading from A0
  totalA0 = totalA0 - readingsA0[index];
  readingsA0[index] = analogRead(ANALOG_PIN_A0);
```

```

totalA0 = totalA0 + readingsA0[index];

// Smooth out the reading from A1
totalA1 = totalA1 - readingsA1[index];
readingsA1[index] = analogRead(ANALOG_PIN_A1);
totalA1 = totalA1 + readingsA1[index];

index = (index + 1) % numReadings;

int smoothedA0 = totalA0 / numReadings;
int smoothedA1 = totalA1 / numReadings;
a= smoothedA1-smoothedA0;
if (a>200)
{
    x=x-1;

}
if (a<200)
{
    x=x+1;

}
analogWrite(PWM_PIN, x); // Example PWM output, not affected by
smoothing

```

```

unsigned long currentMillis = millis();

if (currentMillis - previousMillis >= interval) {
    previousMillis = currentMillis;


    // Toggle between pins 2 and 4
    pwmState = 1 - pwmState;

    // Set the duty cycle based on the current PWM state
    if (pwmState == 0) {
        digitalWrite(2, HIGH); // 50% duty cycle on pin 2
        digitalWrite(4, LOW);   // 0% duty cycle on pin 4
    } else {
        digitalWrite(2, LOW);    // 0% duty cycle on pin 2

```

```
digitalWrite(4, HIGH); // 50% duty cycle on pin 4
}
}
}
```

Output Snaps of our project:

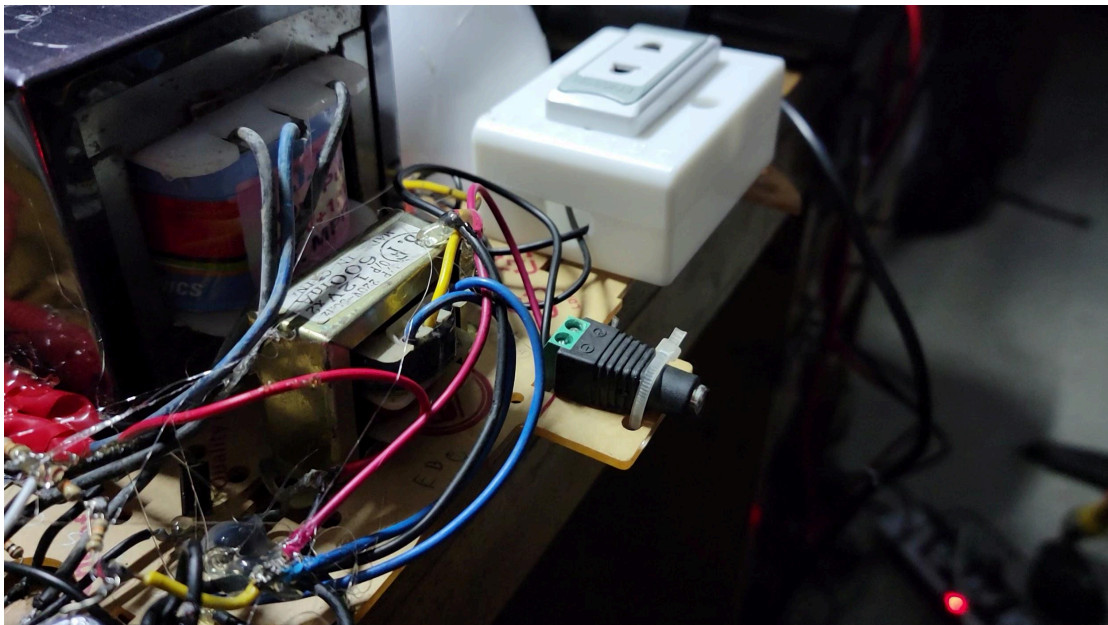





Output Analysis:

In our project's output analysis, we've successfully derived AC output from a DC 12V lithium-ion battery and maintained a constant DC voltage from the input. The significance of this lies in catering to diverse power needs - delivering versatile 230V AC for various devices and a steady 5V DC for USB-compatible devices, all from a singular 12V DC source, typically a battery or solar panel.

For the inverter part, we used a heavy transformer with center tapped coil and the coil ratio was around 1:20. The push pull configuration generated around 210V ac. However the output voltage dropped slightly when any load was connected. Also the output waveshape was a square wave. Both of the shortcomings can be overcome by using SPWM, but that is out of the scope of this project.

For the buck converter feedback part, Two terminals from the output 5V side were run through voltage dividers and to the arduino analog pins. As the project is battery powered, as the battery depletes, the input voltage level will also decrease. To combat this, we measured differential voltage across the terminal, not the voltage with respect to the ground which is floating, in this case. The reason for using a voltage divider is that the arduino cannot take more than 5V as input. So we used a 3:1 voltage divider.

Typical lead acid battery voltage can range from 14V to 11V. Our project is technically capable of taking inputs up to $5 \times 3 = 15V$.

So the low side buck converter has a purpose of two fold. First is that it helps to measure the voltage across the load independent of the ground. Second, it keeps the output voltage stable.

Parts and cost estimations:

Components	Quantity	Cost (BDT)
12V battery	1	1500
Wires		200
Inductor	2	50
Resistors		20
Arduino nano	1	600
N channel Mosfet	5	250
Diode	8	40
12V to 240V step-up transformer		1000
n-p-n transistor	5	250
Breadboard	1	100
Soldering iron and other soldering equipment		500
5W 220V light bulb		150
Small 5V light bulb	2	40
Total		

Discussion:

By doing this project, we were able to learn about the working principles of inverters and buck converters. We gathered practical knowledge about these circuits. However, working with 230V AC was dangerous, so proper precautions were necessary. Also, proper simulations in appropriate software were done to ensure the feasibility of the project. Arduino was used in this project to easily change the generated PWM signals for our desired outputs, which were powered by an external DC source. However, in real life, self-sustaining circuits might be used in place of Arduino, which doesn't require an external power source.

